

## KIRCHHOFF'S LAWS

### OBJECTIVE

To calculate the currents in a multiloop circuit using Ohm's Law and comparing the results to those calculated with Kirchhoff's Current and Voltage Laws

### EQUIPMENT


3 battery packs, circuit board, 2 white shunt connectors, 3 red 75- $\Omega$  resistive connectors, multimeter

### THEORY

- Kirchhoff's Current Law:  $\sum I = 0$  at any node.
- Kirchhoff's Voltage Law:  $\sum V = 0$  around any loop.
- Ohm's Law:  $V = IR$  for any resistor.

### PROCEDURE

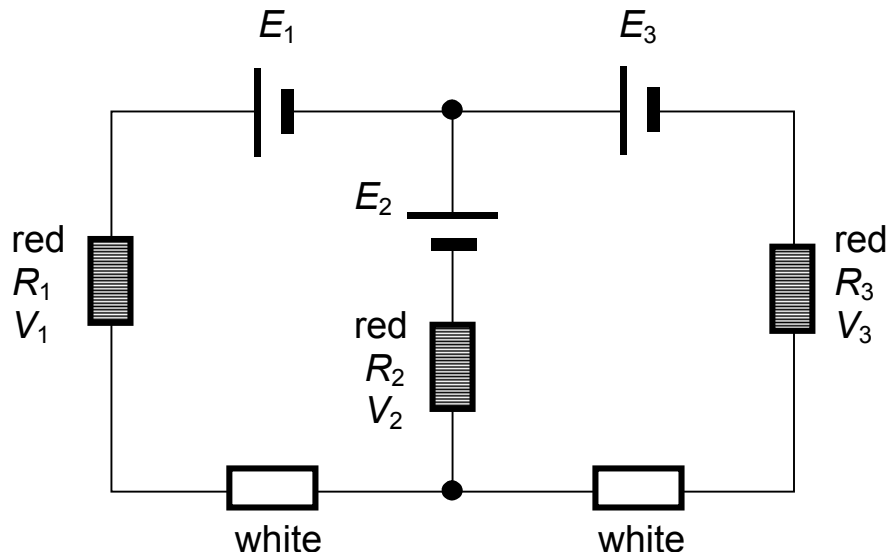- 1) Measure the resistance of each red connector ( $R_1$ ,  $R_2$ ,  $R_3$ ).
- 2) Set up the circuit shown below.
- 3) Measure the terminal voltage across each battery pack ( $E_1$ ,  $E_2$ ,  $E_3$ ) while they are powering the circuit board.
- 4) Measure the voltages across the red connectors ( $V_1$ ,  $V_2$ ,  $V_3$ ) and calculate their currents using Ohm's Law:  $I_1 = V_1/R_1$ ,  $I_2 = V_2/R_2$ ,  $I_3 = V_3/R_3$ .
- 5) Use Kirchhoff's Laws to calculate the currents  $I_1$ ,  $I_2$ , and  $I_3$  using only resistances  $R_1$ ,  $R_2$ ,  $R_3$  and terminal voltages  $E_1$ ,  $E_2$ ,  $E_3$ .
- 6) Compute the percent discrepancy between your results in Steps 4 and 5.



Name \_\_\_\_\_ Date \_\_\_\_\_

Partners \_\_\_\_\_

**KIRCHHOFF'S LAWS DATA SHEET**

Ohm's Law results:

$R_1 = \text{_____ } \Omega$	$V_1 = \text{_____ } V$	$I_1 = \text{_____ } A$
$R_2 = \text{_____ } \Omega$	$V_2 = \text{_____ } V$	$I_2 = \text{_____ } A$
$R_3 = \text{_____ } \Omega$	$V_3 = \text{_____ } V$	$I_3 = \text{_____ } A$

Terminal voltages:

$E_1 = \text{_____ } V$	$E_2 = \text{_____ } V$	$E_3 = \text{_____ } V$
-------------------------	-------------------------	-------------------------

*Show your Kirchhoff's Laws calculations on a separate sheet. Staple it to this sheet when you turn in your work.*

Final Results:

Currents	Ohm's Law	Kirchhoff's Laws	% discrepancy
$I_1$			
$I_2$			
$I_3$			

$$\text{Use \% discrepancy} = \frac{100 \cdot |\text{Meas} - \text{Theo}|}{\text{Theo}}$$

where *Meas* = Ohm's Law currents, and *Theo* = Kirchhoff's Laws currents