

## AMMETERS AND VOLTMETERS

### OBJECTIVE

Electrical devices that measure current and potential difference are called *ammeters* and *voltmeters*, respectively. Often these devices are packed in a single “multimeter” which you have already used in lab. In this experiment you will be building your own ammeter and voltmeter using more fundamental electrical components and the skills you have learned so far in the course.

### THEORY

The basic design criterion of all electrical meters is that they must not significantly disturb the circuit being measured, that is, they must have a negligible effect on all currents and potential differences in the circuit.

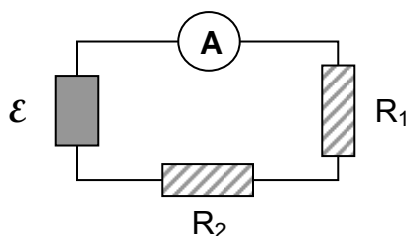


FIGURE 1A

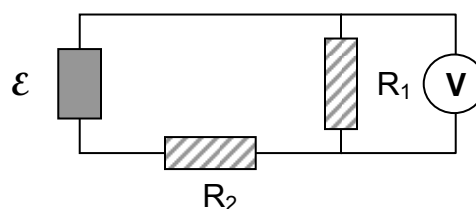


FIGURE 1B

In the series resistive circuit in Figure 1A, the current is being measured by an ammeter placed in series. The ammeter's internal resistance must be much smaller than the resistances  $R_1$  and  $R_2$  in order to insure that the current is not affected by its measurement. In Figure 1B the potential difference across  $R_1$  is being measured by a voltmeter. The voltmeter's internal resistance must be much greater than  $R_1$  in order to prevent a significant amount of current from being diverted into the voltmeter, thereby altering the potential difference.

Before the advent of digital electronics, ammeters and voltmeters were constructed out of simple resistors and galvanometers. A *galvanometer* is a primitive current/potential difference detector. It consists of a coil of wire attached to a rotor inside a permanent magnet. When current flows in the coil, the torque is produced by the magnet's field and the rotor turns and deflects a needle in proportion to the amount of current.

---

### PRE-LAB ACTIVITY

Suppose the circuit in Figure 1 has  $\mathcal{E} = 12 \text{ V}$ ,  $R_1 = 88 \ \Omega$ , and  $R_2 = 125 \ \Omega$ .

1. What is the current in the circuit? Ignore the meters attached.
2. What is the voltage across each resistor? Ignore the meters attached.
3. If the ammeter in Figure 1A has a resistance of  $50 \ \Omega$ , what current does it actually read in the circuit?
4. If the voltmeter in Figure 1B has a resistance of  $150 \ \Omega$ , what voltage does it actually read in the circuit?

**EQUIPMENT**

Galvanometer, 2 decade resistance boxes, adjustable power supply capable of a 5 V output and a current of 500 mA, patch cords, resistance wire

**PROCEDURE****Part 1: Galvanometer Measurements**

We need to measure the internal resistance  $R_g$ , the current  $I_g$  at full-scale deflection, and the voltage  $V_g$  at full-scale deflection.

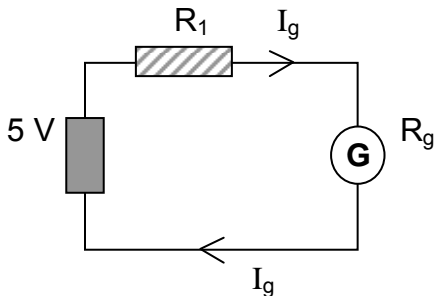


FIGURE 2A


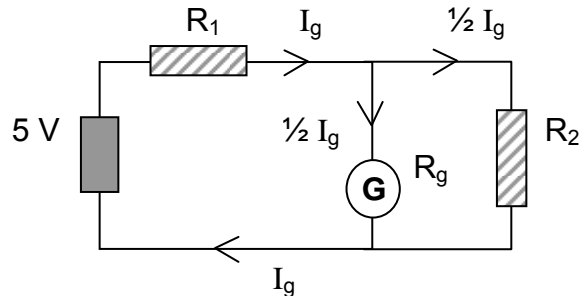


FIGURE 2B

1. Construct the circuit in Figure 2A. Set the decade resistance box  $R_1$  to its highest value before you connect it in the circuit.
2. Slowly decrease  $R_1$  until the needle of the galvanometer deflects full scale. The current  $I_g$  is now flowing in the circuit. Record  $R_1$  on your data sheet.
3. Connect the other decade resistance box  $R_2$  (set to its highest value) in parallel with the galvanometer as shown in Figure 2B.
4. Slowly decrease  $R_2$  until the needle of the galvanometer deflects at half of full scale. Half of  $I_g$  now flows through the galvanometer and through  $R_2$ . Since the voltage across the galvanometer and  $R_2$  is equal,  $R_g = R_2$ . Record this value on your data sheet.
5. Use Ohm's Law to calculate  $I_g$  and  $V_g$  in Figure 2A. Record your results on your data sheet.

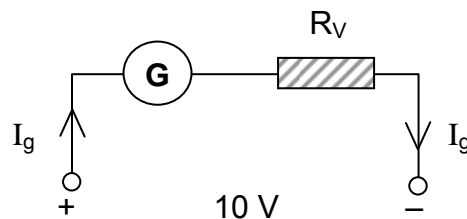**Part 2: Voltmeter Construction**


We wish to construct a dc voltmeter that will achieve full-scale deflection at a maximum of 10 V.



1. Use Kirchhoff's Laws to determine the value of  $R_v$ . Show your work on the data sheet.
2. Construct the circuit shown above. Ask your lab TA to check your work using an adjustable power supply.

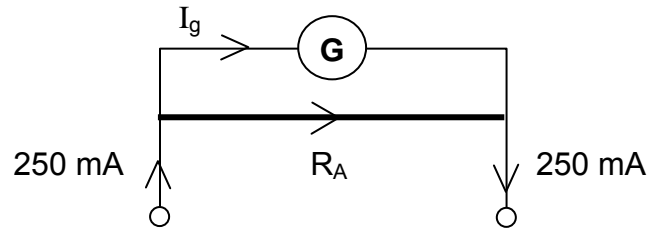**Part 3: Ammeter Construction**

We wish to construct a dc ammeter that will achieve full-scale deflection at a maximum of 250 mA.



1. Use Kirchhoff's Laws to determine the value of R<sub>A</sub>. Show your work on the data sheet.
2. Construct the circuit shown above. You will need to use the resistance wire for R<sub>A</sub> because the required resistance is much smaller than any commercially available resistors. Connect it in parallel with the galvanometer by attaching it directly to its terminals.
3. Connect a known current source to your ammeter. (Your power supply may be able to serve this purpose if it has a variable current knob.) Adjust the length of wire until you achieve full deflection at 250 mA. Ask your lab TA to check your work.
4. **Safety Notice:** Do not leave the resistance wire attached to your current source too long. The wire is a short circuit and may cause your power supply to overheat and malfunction. Also, the wire will get very hot and may cause severe burns.

Name \_\_\_\_\_ Date \_\_\_\_\_

Partners \_\_\_\_\_  
\_\_\_\_\_**AMMETER AND VOLTMETER****Part I: Galvanometer Measurements** $R_g =$  \_\_\_\_\_  $I_g =$  \_\_\_\_\_ $V_g =$  \_\_\_\_\_**Part 2: Voltmeter Construction**

Show your calculations here:

 $R_V =$  \_\_\_\_\_**Part 3: Ammeter Construction**

Show your calculations here:

 $R_A =$  \_\_\_\_\_