

KIRCHHOFF'S LAWS

OBJECTIVE

To calculate the currents in a multiloop circuit using Ohm's Law and comparing the results to those calculated with Kirchhoff's Current and Voltage Laws

EQUIPMENT


3 battery packs, circuit board, 2 white shunt connectors, 3 red 75- Ω resistive connectors, multimeter

THEORY

- Kirchhoff's Current Law: $\Sigma I = 0$ at any node.
- Kirchhoff's Voltage Law: $\Sigma V = 0$ around any loop.
- Ohm's Law: $V = IR$ for any resistor.

PROCEDURE

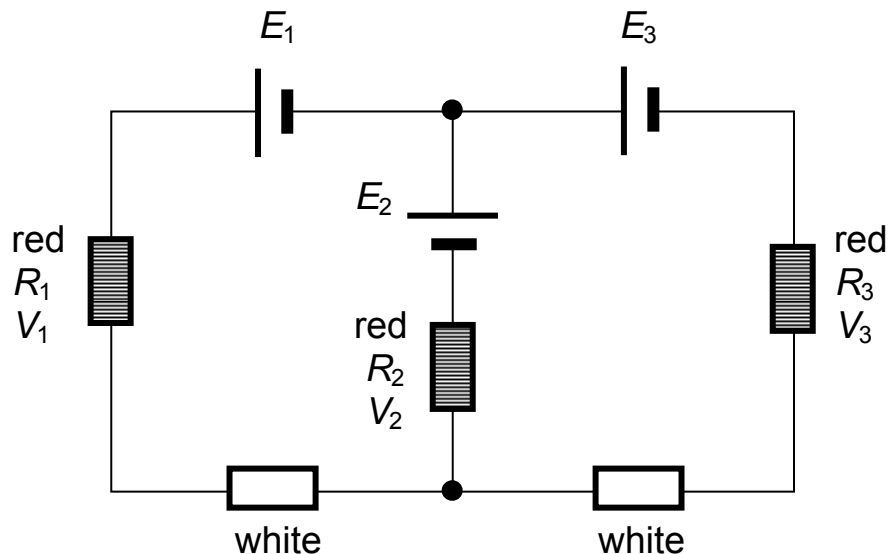- 1) Measure the resistance of each red connector (R_1 , R_2 , R_3).
- 2) Set up the circuit shown below.
- 3) Measure the terminal voltage across each battery pack (E_1 , E_2 , E_3) while they are powering the circuit board.
- 4) Measure the voltages across the red connectors (V_1 , V_2 , V_3) and calculate their currents using Ohm's Law: $I_1 = V_1/R_1$, $I_2 = V_2/R_2$, $I_3 = V_3/R_3$.
- 5) Use Kirchhoff's Laws to calculate the currents I_1 , I_2 , and I_3 using only resistances R_1 , R_2 , R_3 and terminal voltages E_1 , E_2 , E_3 .
- 6) Compute the percent discrepancy between your results in Steps 4 and 5.



Name _____ Date _____

Partners _____
_____**KIRCHHOFF'S LAWS DATA SHEET**

Ohm's Law results:

$R_1 =$ _____ Ω	$V_1 =$ _____ V	$I_1 =$ _____ A
$R_2 =$ _____ Ω	$V_2 =$ _____ V	$I_2 =$ _____ A
$R_3 =$ _____ Ω	$V_3 =$ _____ V	$I_3 =$ _____ A

Terminal voltages:

$E_1 =$ _____ V	$E_2 =$ _____ V	$E_3 =$ _____ V
-----------------	-----------------	-----------------

Show your Kirchhoff's Laws calculations on a separate sheet. Staple it to this sheet when you turn in your work.

Final Results:

Currents	Ohm's Law	Kirchhoff's Laws	% discrepancy
I_1			
I_2			
I_3			

$$\text{Use \% discrepancy} = \frac{100 \cdot |Meas - Theo|}{Theo}$$

where *Meas* = Ohm's Law currents, and *Theo* = Kirchhoff's Laws currents